

VISVESVARAYA TECHNOLOGICAL UNIVERSITY

Jnanasangama, Macche, Santibastwada Road
Belagavi-590018, Karnataka



OPEN ENDED EXPERIMENT

T Flipflops 'And' Gate

Submitted in partial fulfillment of the requirement for the degree of

Bachelor of Engineering – Third Year BE (5th Semester)

in

Electronics & Communication Engineering

by

1DS21EC001

1DS21EC004

1DS21EC006

1DS21EC016

A.Himanshu

Abhijith J Nayak

Abhinav Sundriyal

Aditya K Pawaskar

Under the guidance
of

Dr.P.Vimala, "Professor", ECE Dept
Prof M.Shruti, "Assistant Professor, ECE Dept

Faculty for **VLSI LAB**
(21ECL55)
, DSCE, Bengaluru



Department of Electronics & Communication Engineering
(An Autonomous College affiliated to VTU Belgaum, accredited by NBA & NAAC)
Shavige Malleshwara Hills, Kumaraswamy Layout,
Bengaluru-560078, Karnataka, India

2023-24

Certificate

Certified that the open ended experiment titled “ **T Flipflop ‘And’ Gate** ” carried out by **A.Himanshu(1DS21EC001)**, **Abhijith J Nayak(1DS21EC004)**, **Abhinav Sundriyal (1DS21EC006)**, **Aditya K Pawaskar(1DS21EC016)** are bonafide students of Dayananda Sagar College of Engineering, Bangalore, Karnataka, India in partial fulfillment for the award of Bachelor of Engineering in Electronics & Communication Engineering of the Visvesvaraya Technological University, Belagavi, Karnataka during the academic year 2023-24. This report has been approved as it satisfies the academic requirement in respect of the subject **VLSI LAB** (21ECL55) prescribed for the said degree.

Dr.P.Vimala

M.Shruti

Head of the Department
Dr. T.C.Manjunath

Declaration

Certified that the work entitled, “**T Flipflop ‘And’ Gate**” is a bonafide work that was carried out by ourselves in partial fulfillment for the award of degree of Bachelor of Engineering in Electronics & Communication Engg. of the Visvesvaraya Technological University, Belagavi, Karnataka during the academic year 2023-24. We, hereby declare that the entire work has been done on our own & we have not copied or duplicated any other’s work. The results embedded in this report have not been submitted elsewhere for the award of any type of degree.

Student 1: A. HIMANSHU

USN :1DS21EC001

Sign: _____

Student 2: ABHIJITH J NAYAK

USN: 1DS21EC004

Sign: _____

Student 3: ABHINAV SUNDRIYAL

USN: 1DS21EC006

Sign: _____

Student 4: ADITYA K PAWASKAR

USN: 1DS21EC016

Sign: _____

Date: 29/ 02 /2024

Place: Bengaluru -78

CADENCE VIRTUOSO

- Cadence virtuoso is a very important EDA tool for electronics students learning about IC design/analysis and PCB design/analysis.
- At undergraduate level, virtuoso is majorly used for custom design and analysis of circuits based on MOS technologies, especially in the CMOS VLSI course.
- The Virtuoso System Design Platform allows IC designers to easily include system-level layout parasitic in the IC verification flow, enabling time saving by combining package/board layout connectivity data with the IC layout parasitic electrical model.
- It enables engineers to design concurrently across chip, package, and board, saving time and minimizing errors. It is ideal for designs that integrate multiple heterogeneous ICs, including RF, analog, and digital devices.

Some key benefits of Cadence Virtuoso are:


1. Easy to use, easy to understand software with an interactive interface.
2. Supports circuit design by using symbols and structures in the workspace and also allows textbased design.
3. Great platform for beginners in the core industry to start learning about design and synthesis.
4. Allows the user to analyse the designs on various parameters like power consumption, area usage and delay.

The logo for Cadence, featuring the word "cadence" in a lowercase, bold, sans-serif font. A small red horizontal bar is positioned above the letter "a".

INTRODUCTION


NMOS is a N channel metal oxide semiconductor system. It has P type Substrate and n+ type region in the drain and source. It is used to pass strong logic zero and weak logic 1.

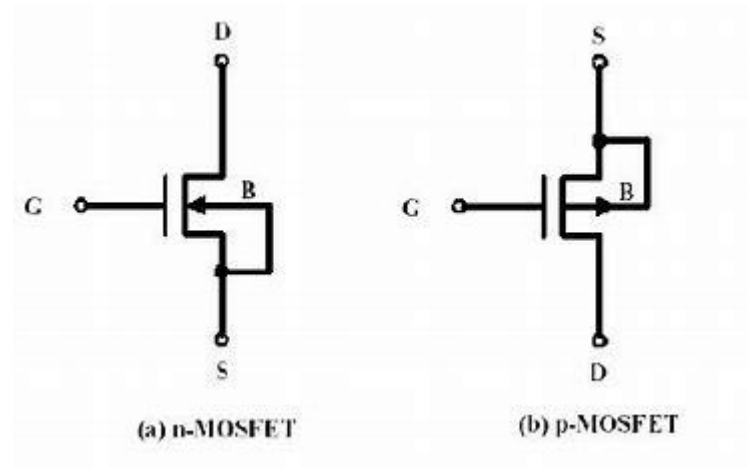PMOS is a P channel metal oxide semiconductor system. It has N type Substrate and p+ type region in the drain and source. It is used to pass strong logic one and weak logic zero.



CMOS is Complementary metal oxide semiconductor system. It uses pair of NMOS and PMOS to design a different logic.

 Below diagram shows CMOS circuit for 2 input NAND gate




T FLIPFLOPS

A T flip-flop, also known as a “Toggle Flip-Flop,” is a fundamental component in the field of digital electronics. It plays a pivotal role in storing and processing binary data, acting as the building block for various digital systems such as counters, shift registers, and memory devices. Essentially, a T flip-flop is a bistable device, which means it has two stable states. It can store one bit of information, either a ‘0’ or a ‘1’. The ‘T’ in T flip-flop stands for “toggle,” which succinctly describes its behavior. When the input or ‘T’ is high (1), the flip-flop toggles its output state. Conversely, when the input is low (0), the output state remains unchanged.

- **Input T (Toggle):** This is the control input of the flip-flop. Depending on its state, the flip-flop either changes or maintains its output.
- **Output Q:** This is the main output which reflects the current state of the flip-flop.
- **Output Q^{bar} :** This is the inverse of the main output Q. If Q is high, Q^{bar} is low, and vice versa.
- **Clock Input:** This input is used to synchronize the flip-flop’s operation with the rest of the digital circuit.


SCHEMATIC OF T FLIPFLOP

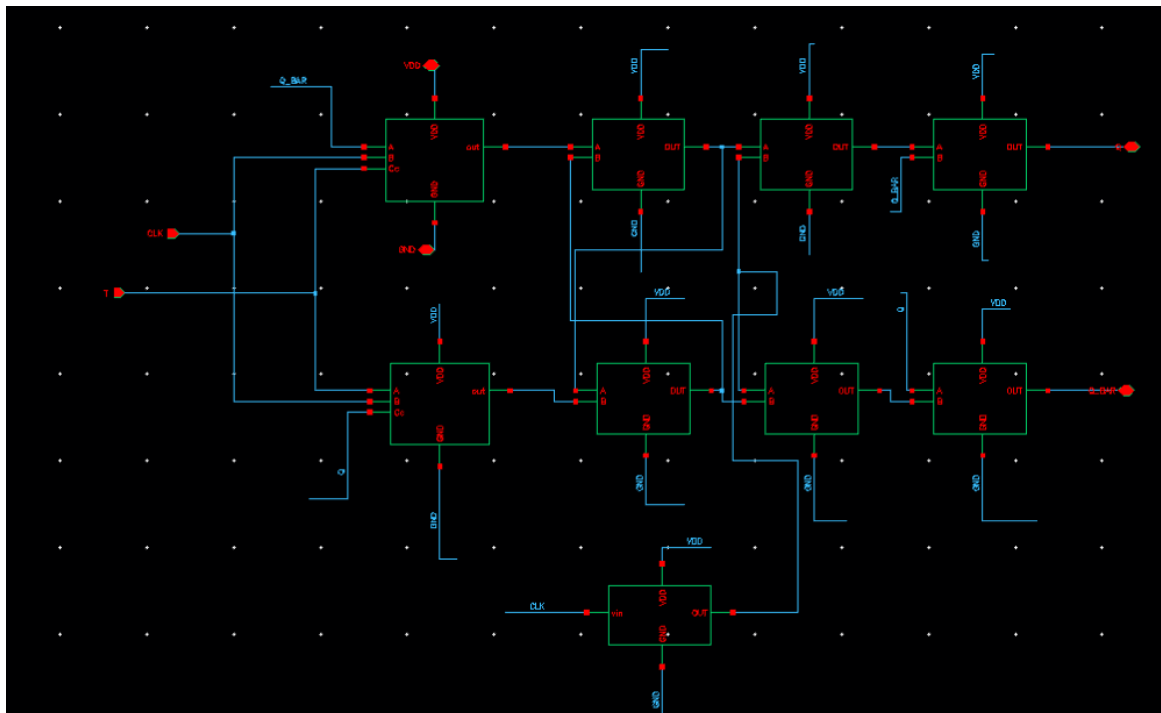


Schematic of T flipflop is done using master-slave JK Flipflops by shorting J and K input and connecting to new input T.

Q and Q_BAR acts as input and output. T and CLK are the input.


SYMBOL

 

TESTING THE CIRCUIT

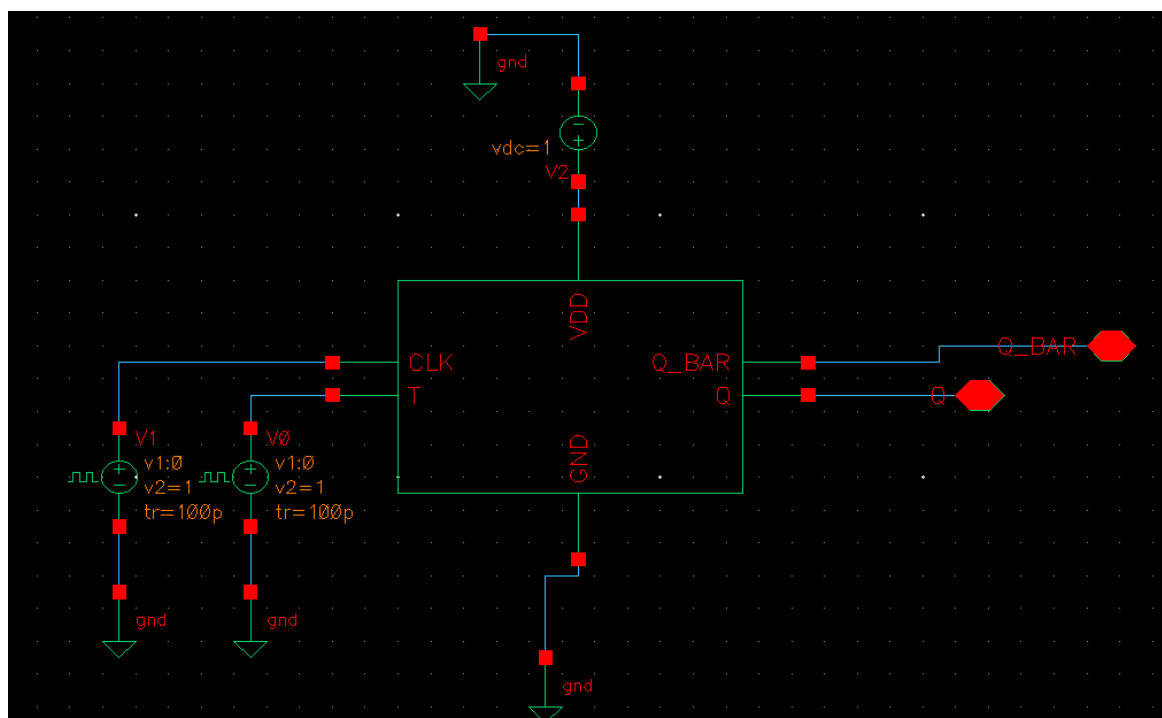

OUTPUT WAVEFORM

 

Transient analysis of T Flipflops

In the above waveform red color waveforms is clock and green color waveform is T input. In the above waveform we can see that, at the start, the flip-flop has an initial state, typically either set or reset, depending on its design. The flip-flop waits for the clock signal to change from high to low that is, it reacts to the falling edge of the clock signal. The flip-flop has an input called T. If T is high (usually logic 1), the flip-flop toggles its output. If T is low (usually logic 0), the output remains unchanged. If T is high at the falling edge of the clock, the flip-flop toggles its output. If T is low, the output remains the same. The flip-flop maintains its output state until the next falling edge of the clock signal occurs.


CONCLUSION

The Cadence simulation of the T Flip Flop has demonstrated its efficiency and reliability. Key parameters such as signal integrity, power consumption, and response time were evaluated. The T Flip Flop exhibited low power consumption, minimal signal distortion, and fast response times, aligning with the design requirements and specifications.

AND GATE

An AND gate is a logic gate having two or more inputs and a single output. An AND gate operates on logical multiplication rules. In this gate, if either of the inputs is low (0), then the output is also low. If all of the inputs are high (1), then the output will also be high. An AND gate can have any number of inputs, although 2 input and 3 input AND gates are the most common.

SYMBOL

 

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

VERILOG CODE

```

module and1(
    input x,y,
    output z
);
    wire z1,n,vdd,gnd;
    assign vdd=1'b1;
    assign gnd=1'b0;
    pmos p1(z1,vdd,x);
    pmos p2(z1,vdd,y);
    nmos n1(n,gnd,x);
    nmos n2(z1,n,y);

    pmos p3(z,vdd,z1);
    nmos n3(z,gnd,z1);
endmodule

```

TESTBENCH

A screenshot of a Verilog code editor window. The window title is "buet@cadence:~/verilog_file". The menu bar includes "File", "Edit", "View", "Search", "Terminal", and "Help". The code is as follows:

```
module and1_tb;
reg x,y;
wire z;
and1 uut(x,y,z);
initial begin
    x=1'b0;y=1'b0;#10;
    x=1'b0;y=1'b1;#10;
    x=1'b1;y=1'b0;#10;
    x=1'b1;y=1'b1;#10;
    $finish;
end
endmodule
```

This are following commands and library used for digital design of And gate
vi cds.lib – It is used to create cds lib for mapping and make the following entries in new tab

DEFINE and1 lib ./and1.lib

mkdir and1.lib – this library creates a work directory for mapping.

vi hdl.var – it creates variable library and we include following command

DEFINE WORK and1_lib


ncvlog and1.v –mess this command is used to compile Verilog code

ncvlog and1_tb.v –mess this command is used to compile Verilog testbench

ncelab and1_tb –access +rwc –mess this is used to read/write access and connectivity.

ncsim and1_tb –gui we use this command to display waveform

OUTPUT WAVEFORMS

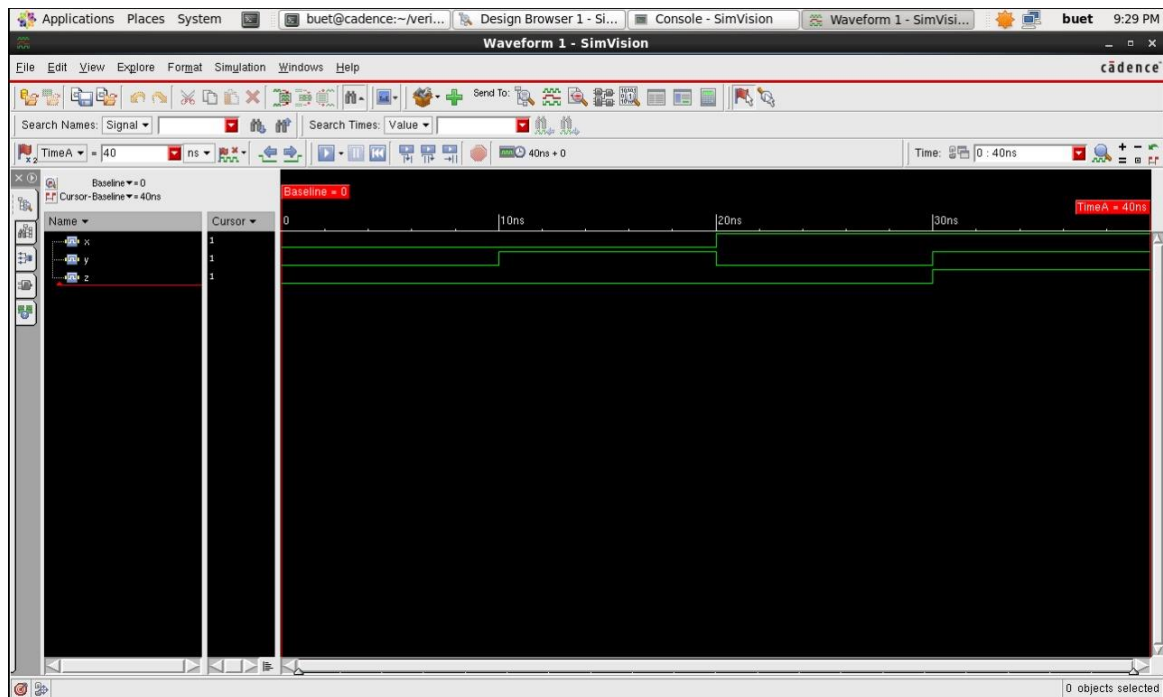

Transient analysis of And gate

From the above waveform we can see that if any of the input A and B is low then output is low(logic 0). If both the inputs are high then output is high(logic 1)

CONCLUSION

The implementation of an AND gate using Verilog in NCSim has been successful. The design process and simulation have deepened our understanding of digital circuits and Verilog. The behavior of the AND gate under various test cases has been insightful.

REFERENCES

[1].

[2]. <https://www.cadence.com/>

[3].

[4]. <https://technobyte.org/verilog-and-gate/>